



OBJECTIVE: This experiment will demonstrate the Arduino **Capacitance Meter and RC Time Constants** project found at <https://www.arduino.cc/en/Tutorial/CapacitanceMeter>.

Parts List

Quantity	ID	Name	Part #
1		Base Grid Base Grid (11" x 7.7")	6SCBG
2	1	1-snap wire	6SC01
3	2	2-snap wire	6SC02
1	3	3-snap wire	6SC03
1	U31	Snapino	6SCU31
1	R1	100 Ω Resistor	6SCR1
1	R4	10K Ω Resistor	6SCR4
1	C3	10 μ F Capacitor (or any other capacitor)	6SCC3
1	J1	Jumper Wire (white)	SCJ3F
1	J5	Jumper Wire (red)	6SCJ5RED
1		USB Cable	9TLSCUSBAB

Step by Step Guide

- 1) Place the upper-left corner of the Snapino at **A4**.
- 2) Snap component **R1** between position **B1** and **B3**.
- 3) Snap component **B2** between position **B8** and **E8**.
- 4) Snap a 1-snap wire at **C3**.
- 5) Snap a 1-snap wire at **E3**.
- 6) Snap a 2-snap wire over the components between **B3** and **B4**.
- 7) Snap a 2-snap wire over the components between **C3** and **C4**.
- 8) Snap a 2-snap wire over the components between **E3** and **E4**.
- 9) Snap a 3-snap wire over the components between **C6** and **E6**.
- 10) Snap the Red Jumper wire over the components between **C6** and **E6**.
- 11) Connect the USB cable between the Snapino and your computer.
- 12) Open the sketch for this project in the Arduino IDE.
- 13) Select **Arduino Genuino/Uno** as the board type.

- 14) Select the COM port for your Snapino.
- 15) Open the **Serial Monitor**.
- 16) Upload the sketch to the Snapino.
- 17) When the upload has completed, watch the output on the Serial Monitor.
- 18) Try various sized capacitors to see if the Snapino can correctly measure their value.
- 19) If some capacitors cannot be measured, try changing the resistor values but do not forget to change the code in the sketch to match the values.

