



OBJECTIVE: This experiment will demonstrate the basic operation of the Snapduino by blinking the LED D1.

### Parts List

Quantity	ID	Name	Part #
1		Base Grid Base Grid (11 x 7.7)	6SCBG
4		2-snap wire	6SC02
1		3-snap wire	6SC03
1		4-snap wire	6SC04
1		5-snap wire	6SC05
1	UA	Snapduino	
1		Snap-FTDI Cable	
1	D1	Red LED	6SCD1
1	R1	100 $\Omega$ Resistor	6SCR1
	S2	Press (Momentary) Switch	6SCS2

### Step by Step Guide

- 1) Snap component **R1** between position **D2** and **D4**.
- 2) Snap component **D1** between **F2** and **F4**.
- 3) Snap a 2-snap wire over the components between **D4** and **D5**.
- 4) Snap a 3-snap wire over the components between **D2** and **F2**.
- 5) Snap a 4-snap wire between **F5** and **F8**.
- 6) Snap a 2-snap wire between **F4** and **F5**.
- 7) Connect the **black** lead of the FTDI cable to the **GND** pin marked with a black ring) on the Snapduino.
- 8) Snap a 2-snap wire over the components between **F5** and **E5**.
- 9) Snap component **S2** between position **B6** and **B8**.
- 10) Snap a 2-snap wire over the components between **B6** and **C6**.
- 11) Connect the **green** lead of the FTDI cable to the 2-snap wire over the **Reset** pin at position C6 on the Snapduino.
- 12) Snap a 5-snap wire over the components between **B8** and **F8**.

### Step by Step Guide *(continued)*

- 13) Connect the **red** lead of the FTDI cable to the **5V** pin (marked with a red ring) on the Snapduino.
- 14) Connect the **yellow** lead of the FTDI cable to the **PB0** pin (marked with a yellow ring) on the Snapduino.
- 15) Connect the **white** lead of the FTDI cable to the **PB1** pin (marked with a white ring) on the Snapduino.
- 16) Open the sketch for this project in the Arduino IDE and upload it to the board.
- 17) When the upload has completed, the red LED will begin to blink.